
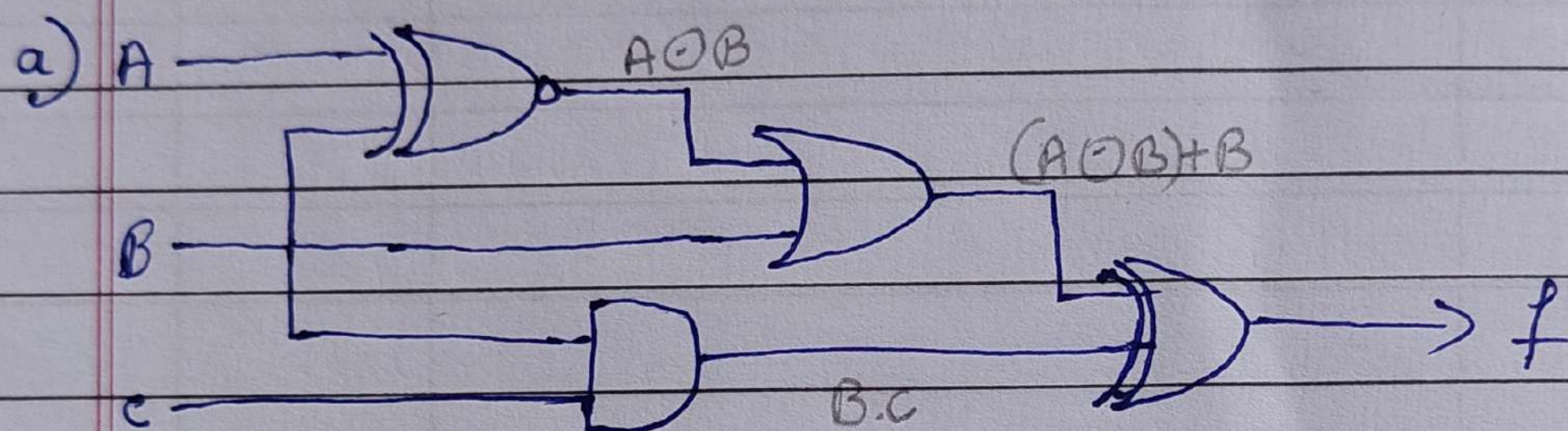


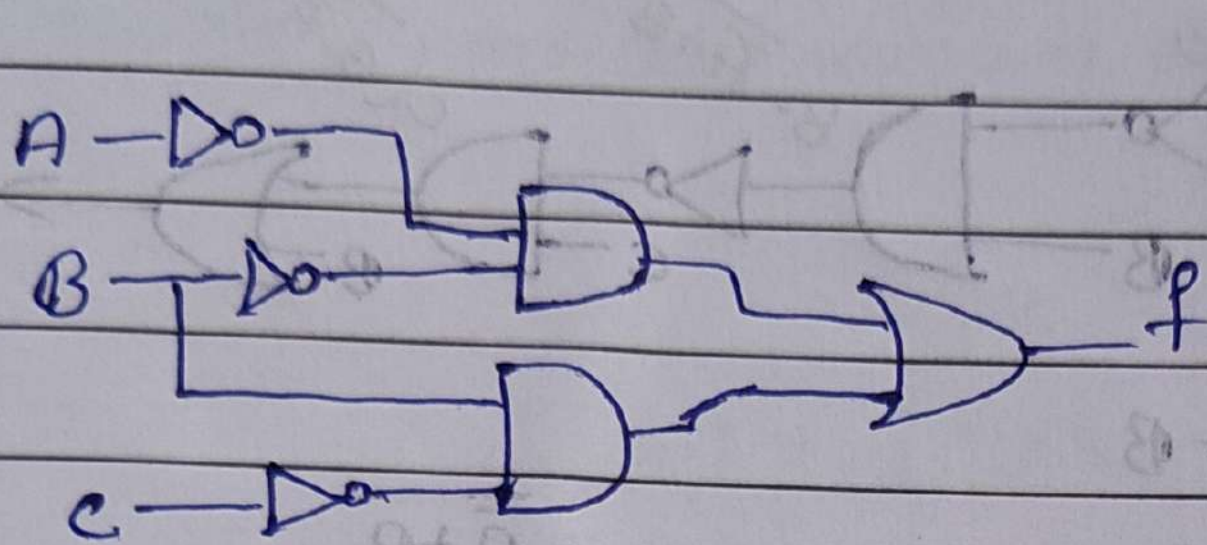1. Derive the output expression 'f' for the below circuits and draw the simplified circuits.



$$\begin{aligned}
 f &= (A \oplus B) \oplus B \oplus B \cdot C \\
 &= AB + \bar{A}\bar{B} + B \oplus BC \\
 &= B(A+1) + \bar{A}\bar{B} \oplus BC \\
 &= B + \bar{B}\bar{A} \oplus BC \\
 &= (B + \bar{B})(B + \bar{A}) \oplus BC \\
 &= (B + \bar{A}) \oplus BC \\
 &= (B + \bar{A})\bar{B}\bar{C} + (\overline{B + \bar{A}})BC \quad 0 \\
 &= (B + \bar{A})(\bar{B} + \bar{C}) + \bar{B}\bar{A}BC \quad 0 \\
 &= 0 + B\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{C} \\
 &\quad \cancel{\bar{A}\bar{B} + \bar{A}\bar{C}} \\
 &= B\bar{C} + \bar{B}\bar{A} + \bar{C}\bar{A} \quad \text{Extra term} \\
 &= B\bar{C} + \bar{B}\bar{A} + \bar{C}\bar{A}(B + \bar{B}) \\
 &= B\bar{C} + \bar{B}\bar{A} + \bar{C}\bar{A}B + \bar{C}\bar{A}\bar{B} \\
 &= B\bar{C}(1 + \bar{A}) + \bar{B}\bar{A}(1 + \bar{C}) \\
 f &= B\bar{C} + \bar{B}\bar{A}
 \end{aligned}$$



$$\overline{B} + \overline{A} =$$

$$\overline{B} + \overline{A} =$$

$$B + ((\overline{B} + \overline{A}) \cdot B) \cdot C = f$$


$$B + (\overline{B} + \overline{A}) \cdot B \cdot C =$$

$$B + (\overline{B} + \overline{A}) \cdot B \cdot C =$$

$$B + (\overline{B} + \overline{A}) \cdot B \cdot C =$$

$$B + \overline{B} \cdot B \cdot C + \overline{A} \cdot B \cdot C = f$$

b)

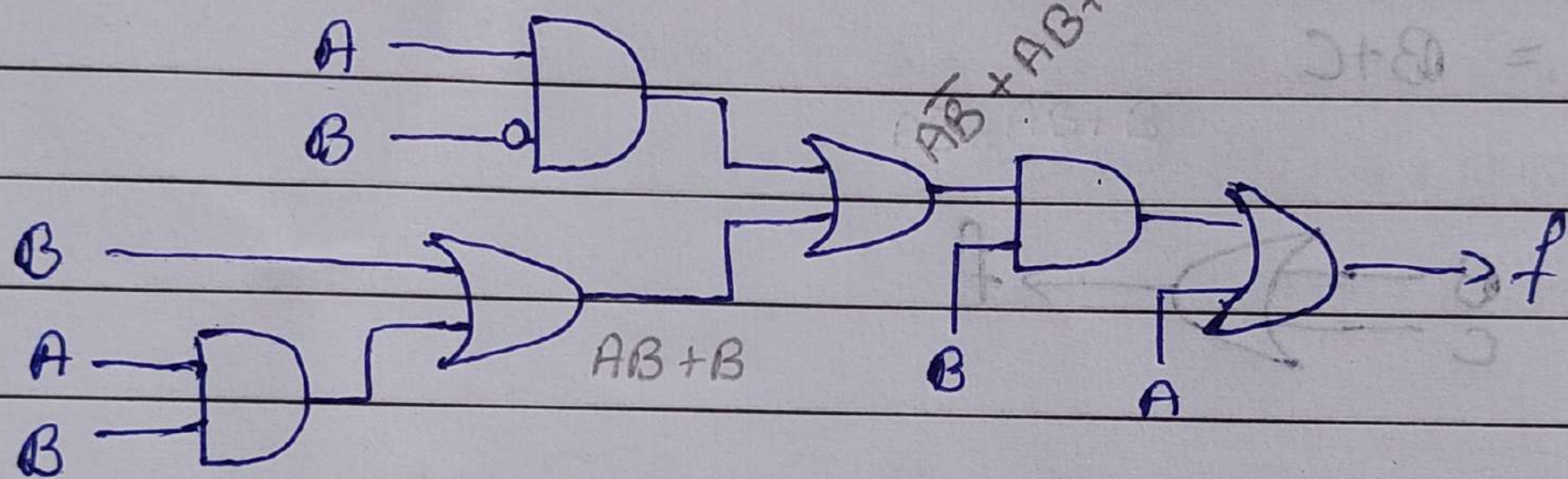


$$f = (A\overline{B} + AB + B) \cdot B + A$$


$$= A\overline{B}B^0 + ABB + BB + A$$

$$= AB + B + A$$

$$= A(B + 1) + B$$

$$f = A + B$$

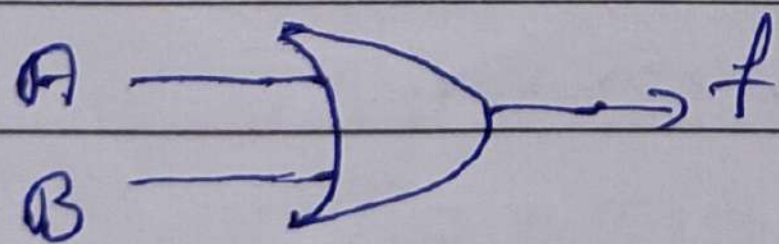

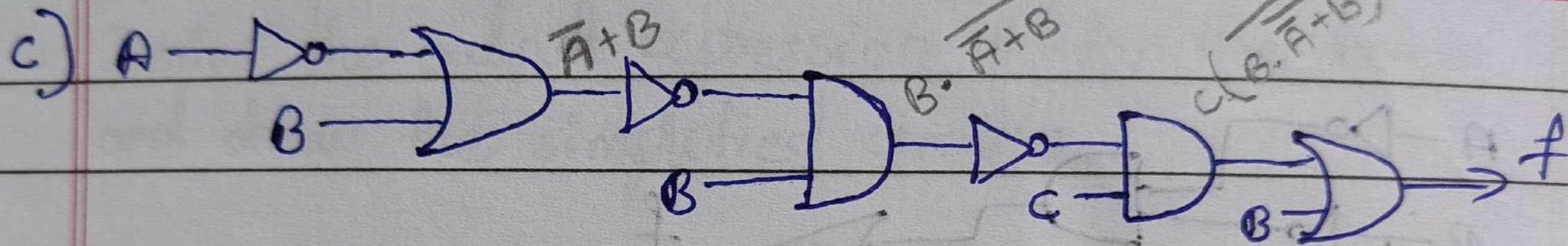

$$f = C \left(\overline{B \cdot (\overline{A+B})} \right) + B$$

$$= C \left(\overline{B \cdot A\bar{B}} \right) + B$$

$$= C \left(\overline{0} \right) + B$$

$$= C(1) + B$$

$$f = B + C$$

$$= \overline{\overline{A+B}}$$

$$= A\bar{B}$$



2. Minimize the following Boolean Expressions using Boolean postulates.

$$\begin{aligned}
 \text{a) } & \bar{A}\bar{C}\bar{D}E + \bar{A}\bar{B}\bar{D} + ABCE + ABD \\
 &= \bar{A}\bar{C}\bar{D}E(B + \bar{B}) + \bar{A}\bar{B}\bar{D} + ABCE(D + \bar{D}) + ABD \\
 &= \bar{A}\bar{C}\bar{D}EB + \bar{A}\bar{C}\bar{D}E\bar{B} + \bar{A}\bar{B}\bar{D} + ABCDE + ABCE\bar{D} + ABD \\
 &= \bar{A}\bar{B}\bar{D}(1 + CE) + \bar{A}\bar{C}\bar{D}EB + ABD(1 + \bar{B}CE) + ABCE\bar{D} \\
 &= \bar{A}\bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}EB + ABD + ABCE\bar{D} \\
 &= ABD + \bar{A}\bar{B}\bar{D} + BC\bar{D}E(A + \bar{A}) \\
 &= ABD + \bar{A}\bar{B}\bar{D} + BC\bar{D}E
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } & \bar{A}\bar{B}\bar{C} + ABD + \bar{A}C + \bar{A}C\bar{D} + A\bar{C}\bar{D} + A\bar{B}\bar{C} \\
 &= \bar{B}\bar{C}(\bar{A} + A) + ABD + \bar{A}C(1 + \bar{D}) + A\bar{C}\bar{D} \\
 &= \bar{B}\bar{C} + ABD + \bar{A}C + A\bar{C}\bar{D} \\
 &= \bar{B}\bar{C} + ABD + \bar{A}C + A\bar{C}\bar{D} \quad \text{Redundant} \\
 &= ABD + \bar{B}\bar{C} + \bar{A}C
 \end{aligned}$$

$$\begin{aligned}
 \text{c) } & \bar{A}\bar{C} + BC + A\bar{B} + \bar{A}BC + A\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \\
 &= \bar{A}\bar{C} + BC(1 + \bar{A}) + A\bar{B} + A\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \\
 &= \bar{A}\bar{C} + BC + A\bar{B} + A\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \\
 &= \bar{A}\bar{C} + \bar{B}\bar{C}\bar{D}A + \bar{B}\bar{C}\bar{D}\bar{A} + BC + A\bar{B} + A\bar{C}\bar{D}B + A\bar{C}\bar{D}\bar{B} \\
 &= \bar{A}\bar{C}(1 + \bar{B}\bar{D}) + \bar{B}\bar{C}\bar{D}A + BC(1 + A\bar{D}) + A\bar{B}(1 + C\bar{D}) \\
 &= \bar{A}\bar{C} + \bar{B}\bar{C}\bar{D}A + BC + A\bar{B} \\
 &= \bar{A}\bar{C} + BC + A\bar{B}(1 + \bar{C}\bar{D})
 \end{aligned}$$

$$\bar{A}\bar{C} + BC + A\bar{B}$$


$$\begin{aligned} d) & \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4 + x_2 \\ & \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_2 (\bar{x}_1 \bar{x}_3 x_4 + 1) \\ & \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + x_2 + \bar{x}_2 \bar{x}_1 x_4 \\ & \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + x_2 + \bar{x}_1 x_4 \end{aligned}$$

$$\bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 + x_3 x_4 + \bar{x}_1 x_3 x_4 + \bar{x}_1 \bar{x}_3 x_4$$

$$\bar{x}_1 \bar{x}_3 (\bar{x}_4 + x_4) + x_2 + x_3 x_4 (1 + \bar{x}_1)$$

$$\bar{x}_1 \bar{x}_3 + x_2 + x_3 x_4$$

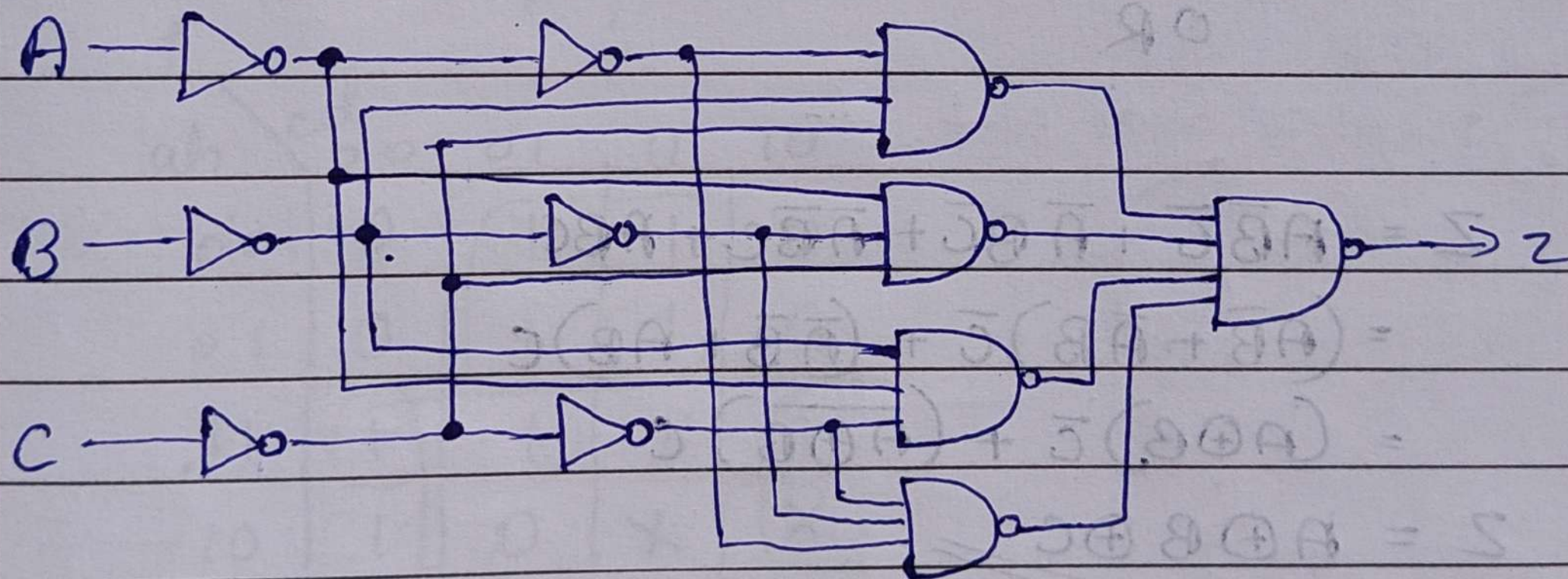3. Which single gate can represent the functionality of given circuit?



$$Z = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}$$

$$Z = \overline{\overline{\bar{A}\bar{B}\bar{C}} \cdot \overline{\bar{A}B\bar{C}} \cdot \overline{\bar{A}\bar{B}C} \cdot \overline{ABC}}$$

$$Z = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

Truth table

A B C Z

0 0 0 0

0 0 1 1

0 1 0 1

0 1 1 0

1 0 0 1

1 0 1 0

1 1 0 0

1 1 1 1

Z is high when odd number
 $\therefore$ it represents XOR gate.

OR

$$Z = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

$$= (\overline{A}\overline{B} + \overline{A}B)\overline{C} + (\overline{A}\overline{B} + AB)C$$

$$= (A \oplus B)\overline{C} + (\overline{A \oplus B})C$$

$$Z = A \oplus B \oplus C$$

3 input XOR gate

4 Minimize the following Boolean Expressions using K-map

a) $f(a, b, c, d) = \sum_m (4, 6, 8, 10, 11, 12, 15) + \sum_d (3, 5, 7, 9)$

ab \ cd	00	01	11	10
00	0	1	X	0
01	1	X	X	1
11	1	1	1	0
10	1	X	1	1

$$f = \bar{a}b + a\bar{b} + cd + b\bar{c}\bar{d} \quad (\text{or } a\bar{c}\bar{b})$$

b) $f(a, b, c, d) = \prod_m (0, 2, 4, 6, 7, 9) \cdot \prod_d (10, 11)$

f \ ab \ cd	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	1	1	1
10	1	0	X	X

$$f = \bar{a}d + ab + a\bar{d}$$